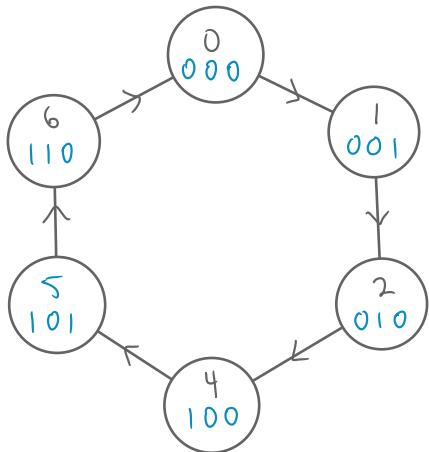


Implement the sequential circuit needed for the following sequence (using T f/f):

$0 \rightarrow 1 \rightarrow 2 \rightarrow 4 \rightarrow 5 \rightarrow 6$




T flip flop Excitation table

| $Q(t)$ | $Q(t+1)$ | T |
|--------|----------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

(d) T

| $Q(t)$ | | | $Q(t+1)$ | | | T _A T _B T _C | | |
|--------|---|---|----------|---|---|--|----------------|----------------|
| A | B | C | A | B | C | T _A | T _B | T _C |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 4 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 5 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 6 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |

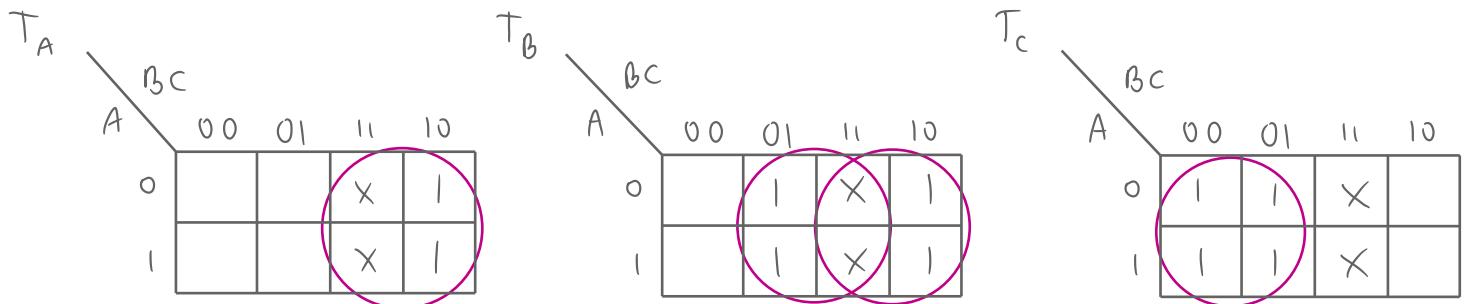


$$T_A = B$$

$$T_B = B + C$$

$$T_C = B'$$

Note: Failure to simplify to the simplest boolean expression can lead to incorrectly determining which states the invalid states transition to, potentially leading to an incorrect conclusion as to whether the circuit is self-correcting or not.

C

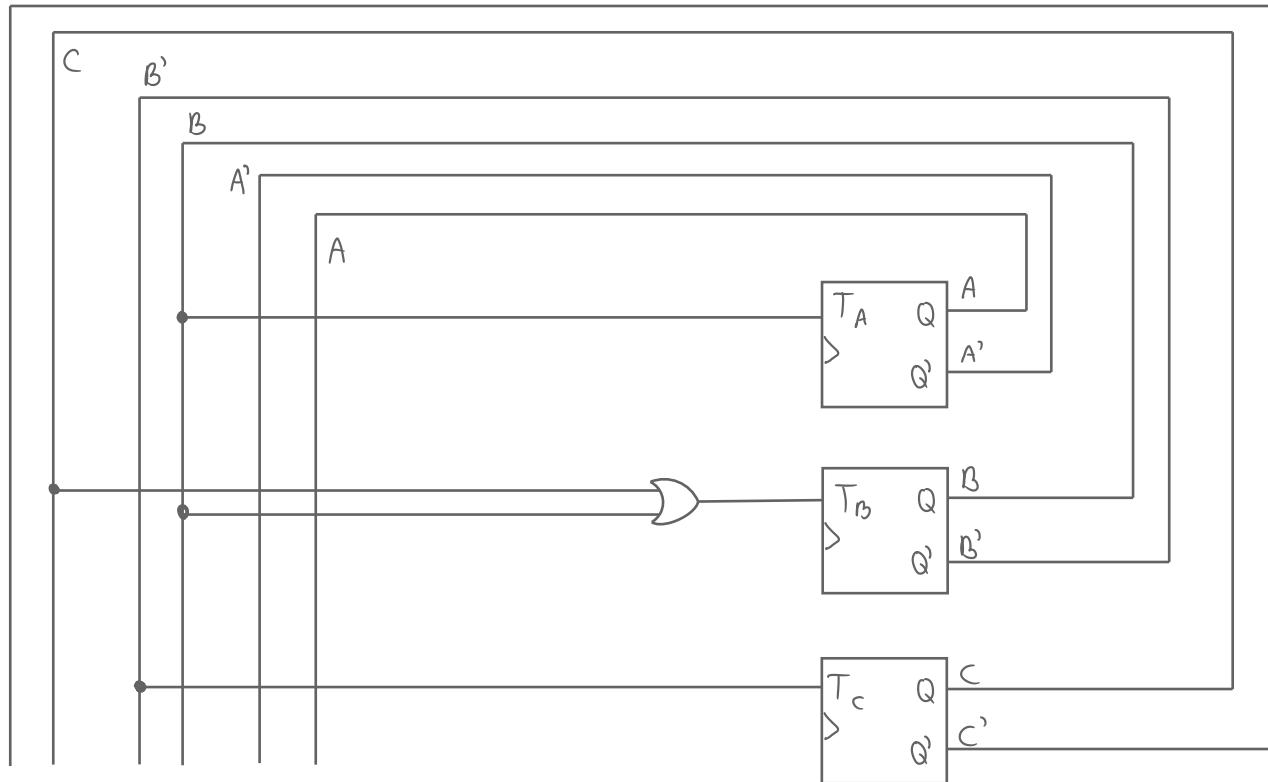

| T | $Q(t+1)$ |
|---|----------|
| 0 | $Q(t)$ |
| 1 | $Q'(t)$ |


T flip flop
characteristic
table

Unused State 011

$$\begin{array}{ccc}
 \begin{array}{ccc} A & B & C \\ 0 & 1 & 1 \\ \downarrow & \downarrow & \downarrow \\ 1 & 0 & 1 \end{array} & T_A = B = 1 \Rightarrow \text{toggle} \\
 & T_B = B + C = 1 + 1 \\
 & \quad = 1 \Rightarrow \text{toggle} \\
 & T_C = B' \\
 & \quad = 0 \Rightarrow \text{no change}
 \end{array}$$

Unused State 111
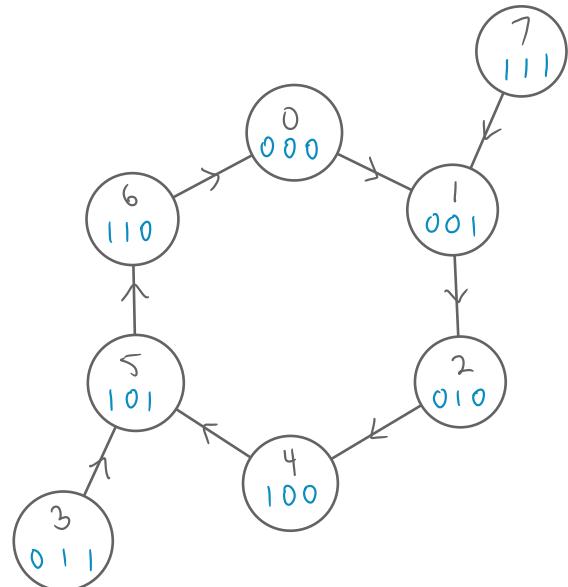
$$\begin{array}{ccc}
 \begin{array}{ccc} A & B & C \\ 1 & 1 & 1 \\ \downarrow & \downarrow & \downarrow \\ 0 & 0 & 1 \end{array} & T_A = B = 1 \Rightarrow \text{toggle} \\
 & T_B = B + C = 1 + 1 \\
 & \quad = 1 \Rightarrow \text{toggle} \\
 & T_C = B' \\
 & \quad = 0 \Rightarrow \text{no change}
 \end{array}$$



Since the invalid states transition to valid states ($011 \rightarrow 100$ and $111 \rightarrow 001$), then this circuit is self correcting.